



UE19EC101#1563#42




SRN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

**PES University, Bangalore**  
(Established under Karnataka Act No. 16 of 2013)

UE19EC101

**DEC 2019: END SEMESTER ASSESSMENT- B.TECH. I SEMESTER**  
**UE19EC101 – Foundation in Electronic Circuits and Systems**

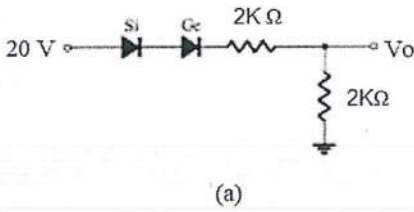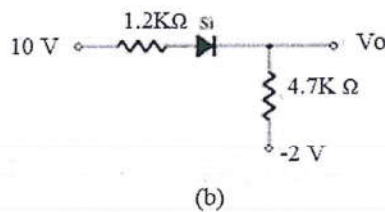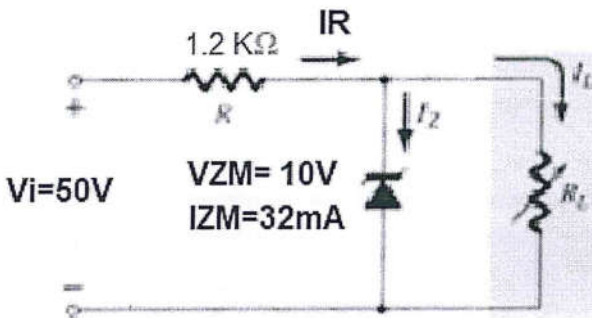Time: 3 hrs		Answer All Questions	Max Marks: 100
1.	a	The Reverse Saturation current of a Si diode is $5 \times 10^{-12}$ A at a temp of 300K. Find the diode current at (i) $40^{\circ}\text{C}$ and a forward voltage of 0.7V (ii) $60^{\circ}\text{C}$ and a forward voltage of 0.7V. Consider ( $\eta=1$ ).	6M
	b	Draw the V-I Characteristics of Semiconductor diode. With the help of the diagram explain three types of Diode Resistance.	6M
	c	Find the Voltage $V_o$ for the series diode configurations circuits shown in the fig (a) and fig (b).  (a)  (b)	8M
2.	a	With a neat diagram and the input and output Waveforms Explain the working of half wave rectifier. Derive the expressions for $V_{dc}$ and $V_{rms}$ . Using these values find the ripple factor $\gamma$ .	7M
	b	Draw full wave Bridge Rectifier circuit with load of $2\text{K}\Omega$ . If the AC voltage applied to the ideal diodes has RMS value of 200V. Calculate (i) Average load current (ii) Average load Voltage. (iii) Ripple voltage. (iv) PIV. (v) RMS voltage.	7 M
	c	For the network shown in the Fig., determine the range of $R_L$ and $I_L$ that will result in $V_{RL}$ being maintained at 10 V. 	6M

3.	a	Simplify the following Expression using Boolean Algebra and realize the same using Basic Gates and NAND gates. (i) $ABC + \bar{A}BC + A\bar{B}C + AB\bar{C}$ (ii) $(AB + \bar{C})(\bar{A} + \bar{B} + C)$	8M
	b	Write the Truth table for Full adder and realize the Circuit using (i) NAND Gates. (ii) Two Half Adders	6M
	c	Write the circuit diagram and Truth Table for the following Digital Sequential circuits. (i) JK Flip flop with Nand gates (ii) Four bit Shift Register ( <b>Consider input as 1101 with initial value of the Register is 0000</b> )	6M
4.	a	Draw and explain the V-I characteristics for the following. Mention the region of operations (i) Output characteristics of Common Emitter Configuration. (ii) Drain Characteristics of n- channel Enhancement MOSFET.	8M
	b	Find $\alpha$ , $I_B$ and $\beta$ for Transistor with $I_C=2.5mA$ and $I_E=2.55mA$ . Find the value of $\beta$ if $\alpha$ is increased by 0.002.	4M
	c	Draw the Block diagram of Communication Systems and explain the characteristics of each block. Discuss frequency reuse concept in cellular system for Mobile communication.	8M
5	a	With a neat block diagram explain the functionality of each building block in embedded systems.	6M
	b	List and explain the different types of Memory supported by embedded systems.	4M
	c	Give the differences between Microprocessor and Microcontroller.	3M
	d	Draw and discuss the data flow model of ARM Processor.	7M