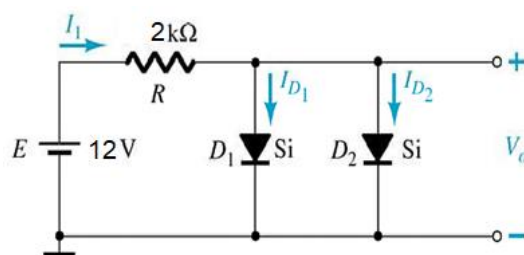
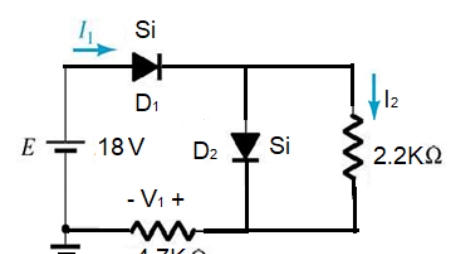
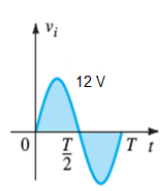
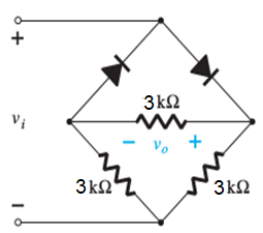
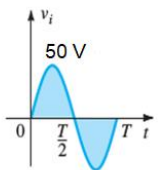
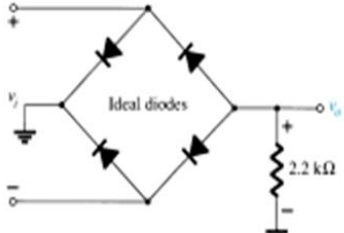
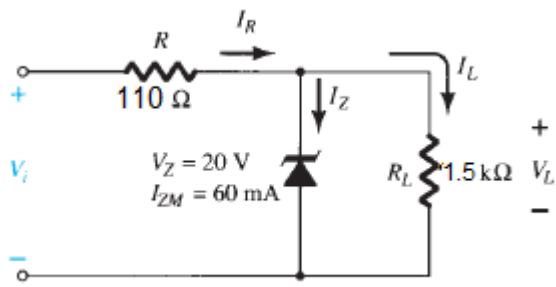
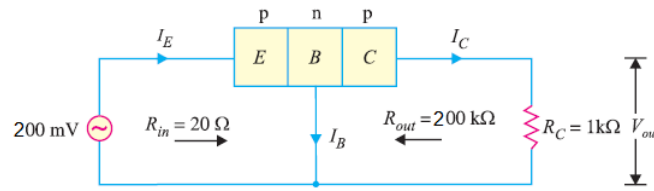


**April 2021: END SEMESTER ASSESSMENT- B.TECH. I SEMESTER**  
**UE20EC101 –Electronic Principles and Devices**

Time: 180 mins		Answer All Questions	Max Marks: 100
1.	a	With a neat circuit diagram Explain Forward and Reverse Characteristics of a semiconductor Diode. Discuss the effect of Temperature on V-I Characteristics.	7M
	b	<p>Solve the following using second approximation for a diode.</p> <p>(i) Determine <math>V_O</math>, <math>I_1</math>, <math>I_{D1}</math>, and <math>I_{D2}</math> for the circuit shown in the Figure below.</p>  <p>(ii) Determine <math>I_1</math>, <math>I_2</math> and <math>V_1</math> for the circuit shown in the Figure below</p> 	7M
	c	Using Shockley's equation, Calculate the applied voltage $V_D$ , if diode current is 5mA, thermal voltage is 26.4 mV and Reverse saturation current is 1.2nA. Consider Ideality factor as 1.	6M
2.	a	For the following Circuits, Determine the output waveform for the network and calculate the output dc level and the required PIV of each diode. Consider Ideal Diodes.	7M
	(i)	<p>(ii)</p> <div style="display: flex; justify-content: space-around; align-items: flex-end;"> <div style="text-align: center;">   </div> <div style="text-align: center;">   </div> </div>	

	<p>b With a neat diagram explain working principle of Full wave Rectifier (centre-Tap) with C filter. Considering <math>500\mu\text{F}</math> capacitor with load current of <math>150\text{mA}</math> at 3% ripple calculate the dc voltage. Assume <math>f=50\text{Hz}</math>.</p>	7M
	<p>c Determine the range of values of <math>V_i</math> that will maintain the Zener diode in the “on” state.</p> 	6M
3.	<p>a Simplify the given Boolean expression and Realize the same using NAND Gates only.  <math>F = XY + X(Y+Z) + Y(Y+Z)</math></p> <p>b Write the Truth Table for Full Adder and Realize the same using          (i) Basic Gates (ii) NAND Gates only.</p> <p>c For the following Sequential Circuits write the Circuit diagram and Characteristic Table          (i) JK Flip Flop          (ii) 4-bit Serial Input Serial Output (SISO) shift register (Consider input 1101).          (iii) 3 bit Asynchronous up-counter</p>	4 M 7 M 9 M
4.	<p>a With a neat diagram explain Input and output V-I characteristics of NPN BJT Common Base Transistor and find the amplification factor for the following Circuit.</p>  <p>b Derive the Expression for Collector Current in terms of <math>\beta</math> and <math>I_{CEO}</math> and Find the value of <math>I_B</math>, <math>\alpha</math> and <math>\beta</math> if <math>I_E = 1.2\text{mA}</math> and <math>I_C = 1.15\text{mA}</math>.</p> <p>c With a neat diagram explain Cellular Communication and describe HAND-OFF strategy.</p>	7M 7M 6 M
5	<p>a List the Characteristics of Embedded System and discuss the types of embedded systems based on Generation.</p> <p>b Give the differences between Microprocessor and Microcontroller</p> <p>c Draw the Data Flow Model of ARM Processor and explain the same.</p>	6M 6M 8M